

Tutorial AN4 (BJT amplifiers)

- For the common-emitter amplifier in Fig. 1, let $V_{CC} = 9\text{ V}$, $R_1 = 27\text{ k}\Omega$, $R_2 = 15\text{ k}\Omega$, $R_E = 1,2\text{ k}\Omega$, and $R_C = 2,2\text{ k}\Omega$. The transistor has $\beta = 100$ and $V_A = 100\text{ V}$. Assume “mid-band” operation i.e. $C_1, C_2, C_E \rightarrow \infty$

Calculate the dc bias currents I_E and I_C . Is the BJT in the active region? If the amplifier operates between a source with $R_{sig} = 10\text{ k}\Omega$ and a load $R_L = 2\text{ k}\Omega$, draw a small-signal equivalent circuit using a π -model for the BJT, and find the values of R_{in} , the voltage gains $A_v \equiv v_o/v_{in}$ and $A_{v sig} \equiv v_o/v_{sig}$ and the current gain $A_i \equiv i_L/i_{in}$.

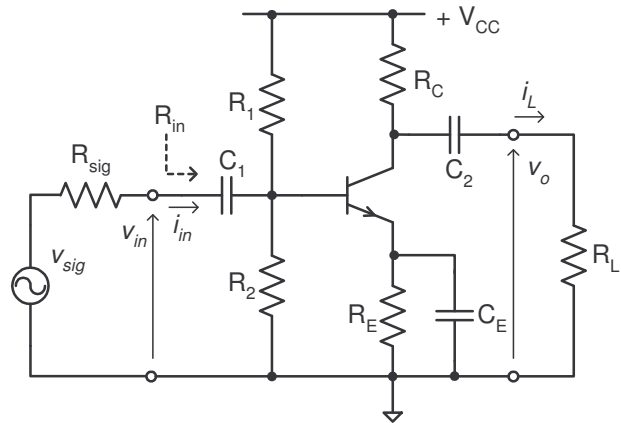


Figure 1

$[I_E = 1,94\text{ mA}; A_v = -78,85\text{ V/V}; A_{v sig} = -8,13\text{ V/V}; A_i = -45,3\text{ A/A}]$

- A designer, having examined the situation described in Q1 and estimating the available gain $A_{v sig}$ to be approximately -8 V/V , wishes to explore the possibility of improvement by reducing the loading of the source by the amplifier input. As an experiment, the designer varies the resistance levels by a factor of approximately 3: R_1 to $82\text{ k}\Omega$, R_2 to $47\text{ k}\Omega$, R_E to $3,6\text{ k}\Omega$, and R_C to $6,8\text{ k}\Omega$. With dc supply voltage, source and load values unchanged, what does the gain become? Comment on the result.

$[A_v = -10,1\text{ V/V}]$

- The amplifier of Fig. 2 consists of two identical common-emitter amplifiers connected in cascade. Observe that the input resistance of the second stage, R_{in2} , constitutes the load resistance of the first stage.

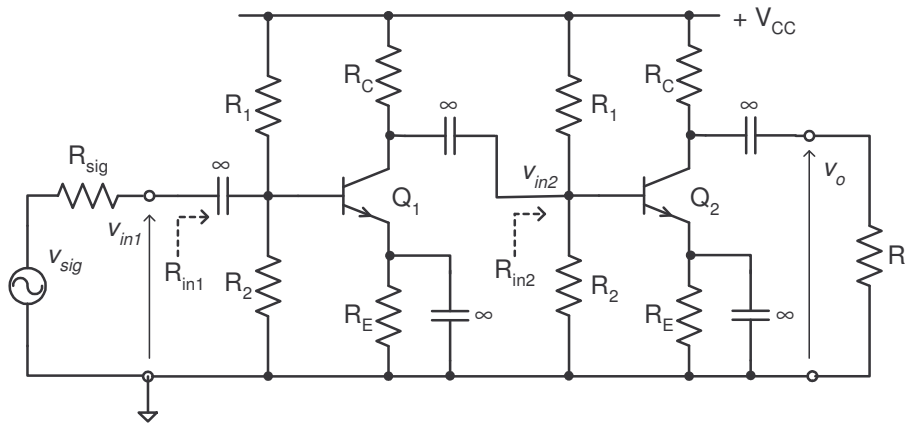


Figure 2

- For $V_{CC} = 15\text{ V}$, $R_1 = 100\text{ k}\Omega$, $R_2 = 47\text{ k}\Omega$, $R_E = 3,9\text{ k}\Omega$, $R_C = 6,8\text{ k}\Omega$, and $\beta = 100$, determine the dc collector current and collector voltage of each transistor.
- Draw the small-signal equivalent circuit of the entire amplifier and give the values of all its components. Neglect r_{o1} and r_{o2} and assume mid-band operation.
- Find R_{in1} and v_{in1}/v_{sig} for $R_{sig} = 5\text{ k}\Omega$.
- Find R_{in2} and $A_{v1} \equiv v_{in2}/v_{in1}$
- For $R_L = 2\text{ k}\Omega$, find $A_{v2} \equiv v_o/v_{in2}$
- Find the overall voltage gain $A_{v sig} \equiv v_o/v_{sig}$

$[I_C = 0,96\text{ mA}; R_{in1} = 2,4\text{ k}\Omega; R_{in2} = 2,4\text{ k}\Omega; A_{v1} = -68,1\text{ V/V}; A_{v2} = -59,3\text{ V/V}; A_{v sig} = 1292\text{ V/V}]$

- 4.1 For the BJT amplifier circuit in Fig. 3, determine the BJT node voltages and V_{CE} , and the currents I_E and I_C in the BJT assuming for the silicon BJT: $V_{BE} = 0,7 \text{ V}$ and $\beta = 150$.

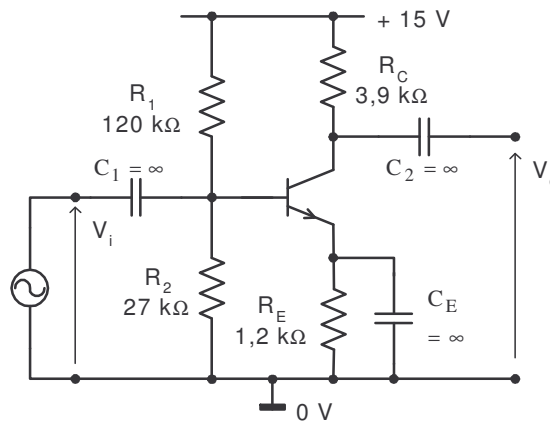


Figure 3

- 4.2 Briefly explain the main advantage of the biasing circuit in Fig. 1 and using the equation for I_E indicate what circuit conditions must be met for this advantage to be realized.
- 4.3 A student *attempts* to connect this circuit as a common emitter amplifier as shown above. She mistakenly omits to connect the emitter bypass capacitor C_E . Draw an ac small-signal equivalent circuit for this amplifier (without C_E) using an appropriate model for the BJT, assuming $V_T = 25 \text{ mV}$ and $V_A = \infty$. Hence determine the voltage gain $A_v = v_o / v_i$, input resistance R_i and output resistance R_o of the amplifier as she connected it.
- 4.4 If C_E had been connected, the voltage gain and input resistance would have been significantly different. Determine the voltage gain and input resistance of the amplifier with C_E connected.
- 4.5 If a load resistance R_L that is much less than R_C is now connected to this amplifier, the voltage gain will be significantly reduced. To minimize this effect, a common collector stage may be added as shown in Fig. 4 below.

1. Assuming $I_{B2} \ll I_{C1}$, determine the emitter current I_{E2} of Q_2 .
2. A load resistance R_L of 600Ω is now connected to the output of the amplifier. Assuming β for Q_2 is 100, determine the input resistance looking into the base of Q_2 with R_L connected, again assuming $V_T = 25 \text{ mV}$ and $V_A = \infty$.
3. Hence determine the overall voltage gain $A_v = v_o / v_i$ of the amplifier with R_L connected.

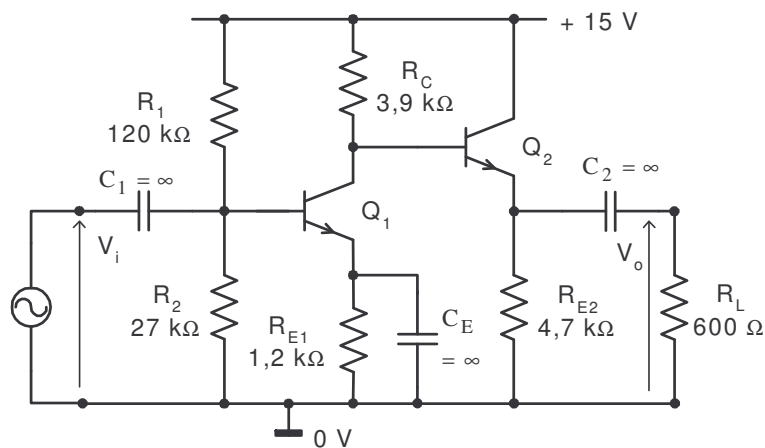


Figure 4